

7. (a) Design the Collpitt's oscillator and explain with help of circuit diagram. Derive the expressions for frequency of oscillation and condition for oscillation, respectively. 6
- (b) Drive the formula $f_t = h_{fe} f_{Hc} f_{Hb}$, where f_t is gain-bandwidth product, h_{fe} is current gain, and f_{Hb} is bandwidth of amplifier in CE configuration respectively. 8
8. (a) Derive expression for current gain in case of amplifier in CE configuration and operated at high frequency (assume output is short circuited). 6
- (b) Draw the circuit diagram of class A transformer coupled power amplifier and compute the conversion efficiency using mathematical analysis. 8
9. (a) Write down difference between tuned amplifier and amplifier having resistive load with help of circuit diagram and transfer functions. 6
- (b) Derive expression for tilt/sag in the output of amplifier acting as high pass circuit (CR circuit) and operated at input step input voltage signal. 8

Code : 041504

4

COPYRIGHT RESERVED

Code : 041504

B.Tech 5th Semester Examination, 2016

Analog Electronics

Time : 3 hours

Full Marks : 70

Instructions :

- (i) *There are Nine Questions in this paper.*
- (ii) *Attempt Five questions in all.*
- (iii) *Question No. 1 is compulsory.*
- (iv) *The marks are indicated in the right-hand margin.*

-
1. Answer the following questions in brief preferably in one/two line (any seven): 2×7=14
- (a) Write two applications of oscillators.
 - (b) Which configuration has highest output impedance in case of equivalent circuit of BJT at low frequency in CE, CB; and CC configuration?
 - (c) In CE amplifier operated at low frequency, what is the phase shift of output current to this input current?
 - (d) List two types of feedback used in the amplifier.
 - (e) What are the Barkhausen criteria for oscillation?

P.T.O.

- (f) Which harmonics are present in the output in case of Class B push-pull power amplifier?
- (g) What is the advantage of CC-CE configuration? $3 \rightarrow$
- (h) What is the advantage of CE-CB configuration? $4 \rightarrow$
- (i) Write down the formula that relates rise time and high cut off frequency in case of amplifier behaving as low pass circuits at higher frequency.
- (j) Write mathematical expression for harmonic distortion.
2. (a) Discuss about ideal voltage amplifiers and ideal current amplifier with diagram and transfer characteristics. 6
- (b) Discuss about frequency and phase distortions, respectively with help of mathematical expressions. 8
3. (a) Write the effect of cascading the CE-CC two stages of amplifiers in term of input impedance, output impedance, current gain and voltage gain over individual stages. 6
- (b) Derive the expression for voltage gain in case of CE amplifier with emitter resistance R_e operated at low frequency. 8

Code : 041504

2

4. (a) Derive expression for upper cut off frequency in case of cascade amplifier, also compute the upper cut off frequency if individual stage upper cut off frequency is 4 MHz and number of cascaded stages are 10. 6
- (b) Derive formula: $t_r = 0.35/f_H$, where t_r is rise time and f_H is high cut off frequency. Above formula needs to be derived for step input applied to the amplifier that is acting as low pass RC circuit at high frequency. 8
5. (a) Write down about any two of the following with help of mathematical expressions. 6
- (i) Thermal noise
- (ii) Shot Noise
- (iii) Flicker noise
- (b) Derive voltage gain for common source FET amplifier operated at low frequency. 8
6. (a) Draw circuit diagram of Wein bridge oscillator and derive the expression for its frequency of oscillation.
- (b) Explain working of class AB power amplifier with help of circuit diagram and also draw its input-output characteristics curve. 8

Code : 041504

3

P.T.O.