

akubihar.com

Code : 041404

B.Tech 4th Semester Examination, 2017

Analog Electronics

Time : 3 hours

Full Marks : 70

Instructions :

- (i) There are Nine Questions in this Paper.
- (ii) Attempt Five questions in all.
- (iii) Question No. 1 is Compulsory. akubihar.com
- (iv) The marks are indicated in the right-hand margin.

1. Answer any seven (7) questions out of ten (10). $2 \times 7 = 14$

- (i) The maximum efficiency of Class B amplifier is:
 - (a) 90%
 - (b) 78.5%
 - (c) 98%
 - (d) 10%
- (ii) Which relationship between the h-parameters is WRONG?
 - (a) $h_{re} = h_{oc}$ akubihar.com
 - (b) $h_{rc} = 1$
 - (c) $h_{re} = h_{rc}$
 - (d) $h_{oc} = 1/h_{re}$
- (iii) Which of the following is the correct values of hybrid- π model parameters (C_c & C_e) at $I_C = 1.3 \text{ mA}$:

akubihar.com

P.T.O.

- (a) 3 pF & 100 pF
- (b) 300 pF & 1 pF
- (c) 30 pF & 10 pF
- (d) 0.03 pF & 1000 pF

akubihar.com

(iv) Which of the following distortion in amplifier result from the production of new frequencies in the output which are not present in the input signal?

- (a) Frequency distortion
- (b) Phase-shift distortion
- (c) Non-linear distortion
- (d) None of these

(v) The input impedance (Z_i) and the output impedance (Z_o) of an ideal trans-conductance (voltage controlled current source) amplifier are:

akubihar.com

- (a) $Z_i = 0, Z_o = 0$
- (b) $Z_i = 0, Z_o = \infty$
- (c) $Z_i = \infty, Z_o = 0$
- (d) $Z_i = \infty, Z_o = \infty$

(vi) Oscillators are working on the principle of:

- (a) Positive feedback
- (b) Negative feedback
- (c) Any of positive or negative feedback
- (d) None of these

akubihar.com

Code : 041404

2

(vii) Impact of current shunt feedback topology is:

- (a) Both input and output resistances decreases
- (b) Both input and output resistances increase
- (c) Input resistance increases, but output resistance decreases
- (d) Input resistance decreases, but output resistance increases

akubihar.com

(viii) Cascading of non-interacting amplifier stages usually results in:

- (a) Increase in overall bandwidth
- (b) Decrease in overall bandwidth
- (c) Decrease in overall gain
- (d) None of these

akubihar.com

(ix) For the feedback amplifier to be stable, its poles must all be in the:

- (a) Left half of the s-plane
- (b) Right half of the s-plane
- (c) Any where in the s-plane
- (d) None of these

(x) For the approximate analysis of low-frequency transistor circuits, two of the four h-parameters (h_{re} and h_{fe}) are sufficient under which of the following condition.

- (a) $h_{re} R_L < 0.1$

akubihar.com

Code : 041404

3

P.T.O.

(b) $h_{re} R_L > 0.1$

(c) $h_{re} = h_{re}$

(d) All of these

akubihar.com

Answer any Four (4) from the remaining Eight (8) Questions.

2. (a) Determine the parameter h_{re} in terms of the CB h-parameters. 6


(b) For the amplifier shown in the figure below. Calculate

$R_i, R_o, A_v, A_{vs}, A_i = \frac{I_2}{I_1}$. Assume $h_{re} = 50$.

$h_{ie} = 1100 \Omega, h_{re} = 24 \times 10^{-4} A/V$, and

$h_{fe} = 2.5 \times 10^{-4}$

akubihar.com

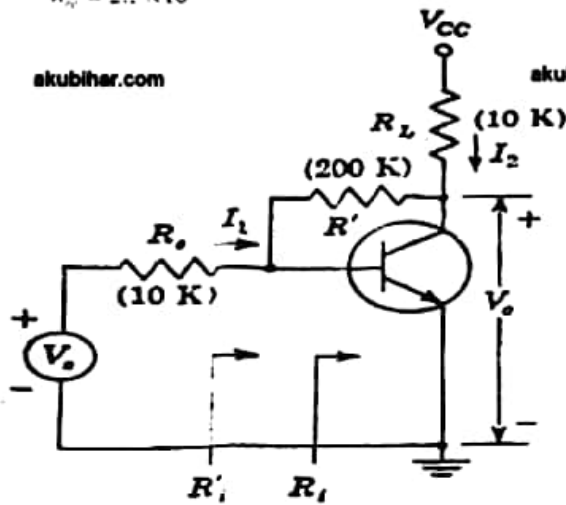

akubihar.com

Code : 041404

4

akubihar.com

3. (a) With the help of suitable figures(s), discuss Trans-resistance amplifier. Determine the expression for its input current, output voltage, and loaded trans-resistance gain. 8

(b) Draw hybrid- π model for a transistor in the CE configuration. Discuss the circuit components. 6

4. (a) Consider an emitter follower. Neglect h_{re} and show that as $R_L \rightarrow \infty$

akubihar.com

(i) $R_i \rightarrow h_{ie} + (1 + h_{fe}) / h_{re} = 1 / h_{re}$

(ii) $1 - AV = h_{re} h_{fe} / (1 + h_{fe})$

Evaluate A_v . Assume $h_{re} = 50, h_{ie} = 1100 \Omega,$

$h_{re} = 24 \times 10^{-4} A/V$, and $h_{fe} = 2.5 \times 10^{-4}$. 7

(b) Describe the Rise time and Tilt (Sag).

Find the rise time for an amplifier with 1 MHz bandpass.

Also, find the per cent tilt, if we wish to pass a 50-Hz square wave with lower 3-dB frequency of 10 Hz. 7


5. (a) A two-stage FET RC-coupled amplifier has the following parameters: $g_m = 10 \text{ mA/V}, r_d = 5.5 \text{ k}\Omega, R_d = 10 \text{ k}\Omega$ and $R_g = 0.5 \text{ M}\Omega$ for each stage. Assume C_1 in the figure below to be arbitrarily large. (i) What must be the value of C_2 in order that the frequency characteristics of each stage be flat within 1 dB down to 10 Hz? (ii) repeat part (i) if the overall gain of both stages is to be down 1 dB at 10 Hz? (iii) What is the overall mid-band voltage gain?

Code : 041404

5

akubihar.com

P.T.O.

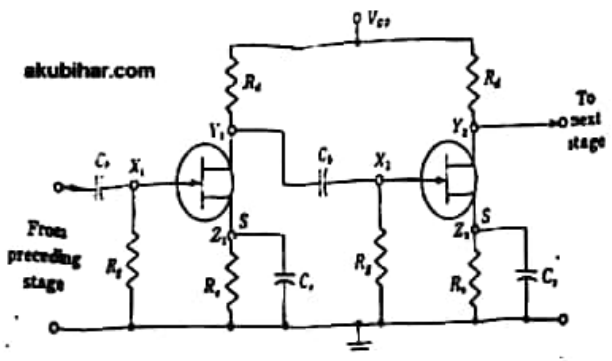

- (b) Sketch the circuit of a push-pull class B transistor amplifier in the common-collector configuration without an output transformer. akubihar.com 2
6. (a) Derive the expression for the CE short-circuit current gain A as a function of frequency. 7
- (b) Given the following transistor measurements made at $I_C = 5\text{mA}$, $V_{CE} = 10\text{V}$, and at room temperature; $h_{fe} = 100$, $h_{ie} = 600\text{ohms}$, $[A_{v_{mid}}] = 10$ at 10MHz , $C_c = 3\text{pF}$. Find f_{β} , f_T , C_c , r_{be} , r_b , b . The symbols used have their usual meaning.
7. (a) Define and discuss the positive feedback. Also give two *Barkhausen conditions* required in order for sinusoidal oscillations to be sustained. 7

akubihar.com
Code : 041404 6

- (b) Discuss the classification of amplifiers according to method of operations. akubihar.com 7
8. (a) With the help of suitable diagram(s), describe the Wien bridge oscillator. 7
- (b) An amplifier with an open-loop voltage gain of 1000 delivers 10 W of output power at 10 per cent second-harmonic distortion when the input signal is 10 mV. If 40-dB negative-series feedback is applied and the output power is to remain at 10 W, determine (i) the required input signal, (ii) the per cent harmonic distortion. 7
9. (a) Design a phase-shift oscillator to operate at a frequency of 5 kHz. Use a MOSFET with $\mu = 55$ and $r_d = 5.5\text{K}$. The phase-shift network is not to load down the amplifier. (i) Find the minimum value of the drain-circuit resistance R_d for which the circuit will oscillate, (ii) Find the product RC, (iii) Choose a reasonable value for R, and find C. 9
- (b) With the help of suitable diagram(s), discuss the Tuned amplifier. 5

akubihar.com

Code :041404 7