

Code : 041504

B.Tech 5th Semester Exam., 2018

ANALOG ELECTRONICS

Time : 3 hours

Full Marks : 70

Instructions:

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Choose the correct answer (any seven) : $2 \times 7 = 14$

(a) For the BJT circuit (Fig. 1) shown below, assume that the β of the transistor is very large and $V_{BE} = 0.7 \text{ V}$:

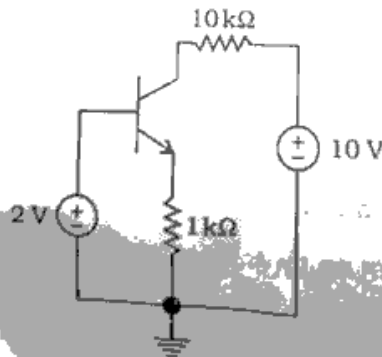


Fig. 1

http://www.akubihar.com

http://www.akubihar.com

(4)

(e) The small-signal gain of the amplifier V_C/V_S is

- (i) -10
- (ii) -5.3
- (iii) 5.3
- (iv) 10

(f) The value of C required for sinusoidal oscillations of frequency 1 kHz in the circuit shown in Fig. 4 is

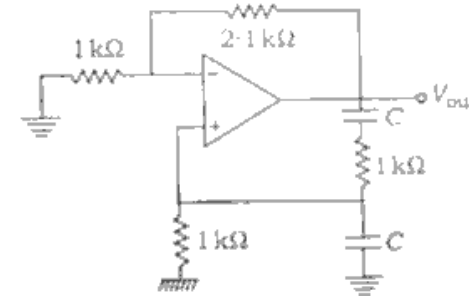


Fig. 4

- (i) $\frac{1}{2\pi} \mu\text{F}$
- (ii) $2\pi \mu\text{F}$
- (iii) $\frac{1}{2\pi\sqrt{6}} \mu\text{F}$
- (iv) $2\pi\sqrt{6} \mu\text{F}$

$f = \frac{1}{2\pi RC}$
 $2\pi RC = \frac{1}{f}$
 $C = \frac{1}{2\pi R f}$
 $C = \frac{1}{2\pi \times 1000 \times 1000}$
 $C = \frac{1}{2\pi \times 10^6}$
 $C = \frac{1}{2\pi\sqrt{6} \times 10^6}$
 $C = \frac{1}{2\pi\sqrt{6}} \mu\text{F}$

http://www.akubihar.com

http://www.akubihar.com

(2)

The mode of operation of the BJT is

- (i) cut-off
- (ii) saturation
- (iii) normal active ✓
- (iv) reverse active

(b) Assuming $V_{CE, \text{sat}} = 0.2 \text{ V}$ and $\beta = 50$, the minimum base current (I_B) required to drive the transistor in the given figure (Fig. 2) to saturation is

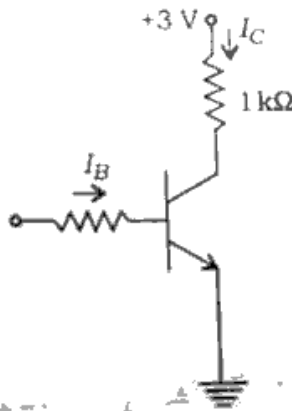


Fig. 2

- (i) $56 \mu\text{A}$
- (ii) $140 \mu\text{A}$
- (iii) 60 mA
- ✓ (iv) 3 mA

(6)

(i) In Fig. 4, transconductance in millisiemens (mS) and voltage gain of the amplifier are, respectively

- (i) 1.875 mS and 3.41
- (ii) 1.875 mS and -3.41
- (iii) 3.3 mS and -6
- (iv) 3.3 mS and 6

(j) The cascade amplifier is a multistage configuration of

- (i) CC-CB
- (ii) CE-CB
- (iii) CB-CC ✓
- (iv) CE-CC ⊗

2. (a) Explain class B transformer-coupled amplifier with circuit diagram.

(b) A transformer-coupled class A amplifier supply

(3)

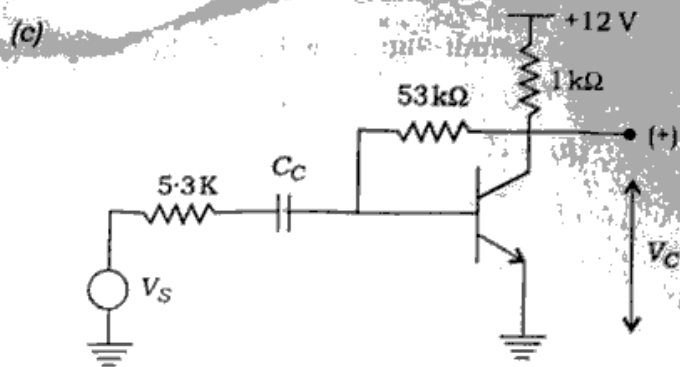


Fig. 3

In the transistor amplifier circuit shown in Fig. 3 the transistor has the following parameters :

$\beta_{DC} = 60, V_{BE} = 0.7 \text{ V}, h_{ie} = \alpha, h_{fe} = \alpha$

The capacitance C_C can be assumed to be infinite. Under DC conditions, the collector to emitter voltage drop is

- (i) 4.8 V ✓
- (ii) 5.3 V
- (iii) 6 V
- (iv) 6.6 V

(d) In Fig. 3, if β_{DC} is increased by 10%, then collector to emitter voltage drop

- (i) increases by less than or equal to 10%
- (ii) decreases by less than or equal to 10%
- (iii) increases by more than 10%
- (iv) decreases by more than 10%

(5)

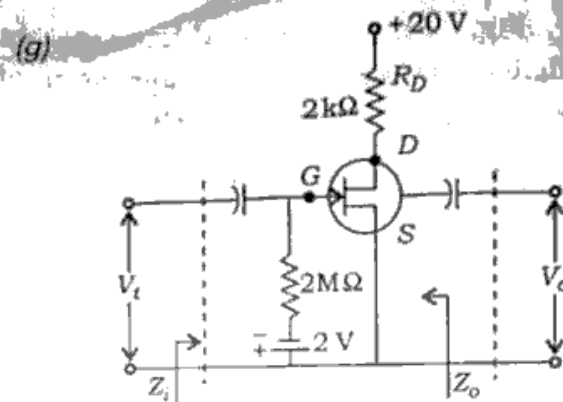


Fig. 5

Given $r_d = 20 \text{ k}\Omega, I_{DSS} = 10 \text{ mA}, V_P = -8 \text{ V}, Z_i$ and Z_o of the circuit are, respectively

- (i) 2 MΩ and 2 kΩ
- (ii) 2 MΩ and $\frac{20}{11} \text{ k}\Omega$
- (iii) infinity and 2 kΩ
- (iv) infinity and $\frac{20}{11} \text{ k}\Omega$ ✓

(h) I_D and V_{DS} in Fig. 4 under DC conditions are, respectively

- (i) 5.625 mA and 8.75 V
- (ii) 7.5 mA and 5 V
- (iii) 4.5 mA and 11 V
- (iv) 6.250 mA and 7.5 V

... oscillator with circuit diagram.

- (b) In a BJT-based R-C phase-shift oscillator, $R = 200 \text{ k}\Omega$, $C = 200 \text{ PF}$. Find the frequency of the BJT-based oscillator. 7+7=14

4.

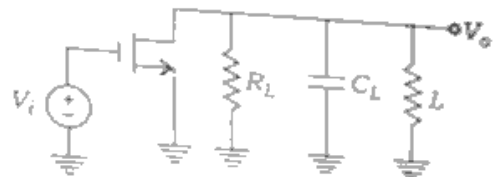


Fig. 6

It is required to design a tuned amplifier of the type shown in Fig. 6, having $f_0 = 1 \text{ MHz}$, 3 dB bandwidth = 10 kHz, centre frequency gain = -10 V/V. The FET available has at the bias point $g_m = 5 \text{ mA/V}$ and $r_0 = 10 \text{ k}\Omega$. The output capacitance is negligibly small. Determine R_L , C_L and L .

14

5. Draw the small-signal equivalent circuit of common-emitter amplifier and derive the expression for (a) current gain, (b) input resistance and (c) voltage gain. 14

6. Draw the hybrid- π model for a transistor in the CE configuration and discuss about each parameter. 14

AK9/147

(Turn Over)

(8)

7. Explain the effect of an emitter bypass capacitor on low frequency response of a BJT-based basic amplifier. 14

8. Explain the operation of common-base configuration of BJT and draw the input-output characteristics. Also explain the early effect. 14

9. Write short notes on the following : 7+7=14
 (a) Ideal voltage amplifier
 (b) Ideal transconductance amplifier

http://www.akubihar.com

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से