

B.Tech 5th Semester Exam., 2019

ANALOG ELECTRONICS

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer any seven of the following questions briefly : 2×7=14

- (a) The ear is not sensitive to which type of distortion in the amplifier?
- (b) Write the condition for approximate model of BJT in CE configuration.
- (c) What is the phase difference between input and output currents in CE configuration?
- (d) Why is the Bootstrap principle used in emitter follower circuit?
- (e) What is Gain Bandwidth Product?

- (f) Which of the BJT transistor currents is always the largest?
- (g) What are the main purposes for which a CC amplifier may be used?
- (h) What is the purpose of transformer coupling in transistor amplifier?
- (i) Why is CB amplifier used as constant current source?
- (j) Explain the Barkhausen criterion.

2. (a) Explain the phase distortion in amplifier and list the various causes for distortion.

(b) Draw the approximate small-signal equivalent circuit at low frequency for common-base amplifier with load resistance R_L . Compute the output resistance in terms of h parameter.

6+8=14

3. (a) The BJT is connected as a CE amplifier. Determine Z_i , Z_o , A_I and A_V using complete hybrid model.

(b) For an emitter bias BJT circuit (capacitor is bypassed), determine r_e , Z_i , Z_o and A_V . Given :

$$R_B = 470 \text{ k}\Omega, R_C = 2.2 \text{ k}\Omega, V_{CC} = 20 \text{ V}$$


$$R_E = 0.56 \text{ k}\Omega, C_E = 10 \mu\text{F}, \beta = 120,$$

$$r_o = 40 \text{ k}\Omega, C_c = 10 \mu\text{F}$$

7+7=14

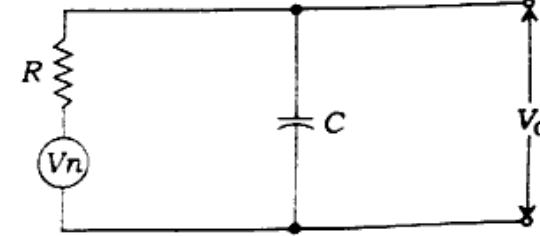4. (a) Draw the single stage RC coupled BJT amplifier and discuss the effect of (i) input capacitance C_s , (ii) emitter bypass capacitor C_e and (iii) output capacitor C_c , on the frequency response.
- (b) Derive an expression for percentage tilt (P) in the output waveform for square symmetrical wave applied as input to an amplifier that behaves as high-pass circuit at low-frequency signal. 8+6=14
5. (a) Derive the expressions for input and output resistances in case of emitter follower BJT amplifier using its hybrid model. <http://www.akubihar.com>
- (b) Derive the expressions for voltage gain in case of low-frequency common-drain FET amplifier and prove why voltage gain is less than unity. 8+6=14
6. (a) Find the mean-square value V_0^2 of the output noise voltage for the circuit shown in the figure given below. The circuit represents a generator

supplying Johnson noise to the RC combination. Prove that $\frac{1}{2} CV_0^2 = \frac{1}{2} kT$:



- (b) Compute overall lower 3-dB frequency for four interacting stages amplifier having individual stage lower 3-dB frequency, $f_1 = 40$ Hz, $f_2 = 100$ Hz, $f_3 = 50$ Hz and $f_4 = 10$ Hz. 9+5=14
7. (a) With a neat circuit diagram, explain the operation of a transformer coupled class A power amplifier.
- (b) Compute the expression for current gain using small-signal equivalent circuit at high frequency for common-drain FET amplifier with load resistance R_L . 6+8=14
8. (a) Derive the relationship between t_p and high 3-dB frequency f_H in order to amplify the pulse without excessive distortion.

- (b) Derive the frequency and condition of oscillation for FET phase-shift oscillator.

7+7=14

9. (a) Explain the working of a class B push pull amplifier. Prove that the maximum efficiency is 78.5%.

- (b) Derive the expressions for frequency and condition of oscillation in case of Wien bridge oscillator. Determine the maximum and minimum frequency of oscillations of a Wien bridge oscillator circuit having a resistor of 10 k Ω and a variable capacitor of 1 nF to 1000 nF.

7+7=14

http://www.akubihar.com

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से

20AK—2580/348

Code : 041504

http://www.akubihar.com